

TPS61150 Dual Output Boost Converter to Drive up to 14 WLEDs, Keypad, and LCD Backlight

*Sahana Chandra**PMP Portable Power*

ABSTRACT

The TPS61150/1 is a high-frequency boost converter with two regulated current outputs for driving white light-emitting diodes (WLED). The reference design and applications examples in this document show the TPS61150 driving up to 14 WLEDs, a keypad, and a LCD backlight application. The two current outputs are ideal for driving WLED backlight for the sub and main displays in clamshell phones.

1 Features

- 3 V to 6 V Input Voltage Range
- Two Outputs Each up to 27 V
- 0.7 A Integrated Switch
- Built-in Power Diode
- 1.2 MHz Fixed PWM Frequency
- Individually Programmable Output Current
- Input-to-Output Isolation
- Built-in Soft Start
- Overvoltage Protection
- Up to 83% Efficiency
- Up to 30 kHz PWM Dimming Frequency
- Available in a 10 Pin, 3 × 3 mm QFN Package

2 TPS61150 Reference Design

The reference design contains a TPS61150 IC and supports passives which provide two independently regulated output currents using a single inductor step-up boost converter. One output drives two parallel strings of WLEDs. One string can be configured for two or four series WLEDs. The other string has four series WLEDs.

The TPS61151 IC has the same pinout as the TPS61150; the only difference is the overvoltage protection (OVP) at 28 V for the TPS61150 and 22 V for the TPS61151. Therefore, they can be switched out and used on the same board.

3 TPS61150 Schematic and Bill of Materials

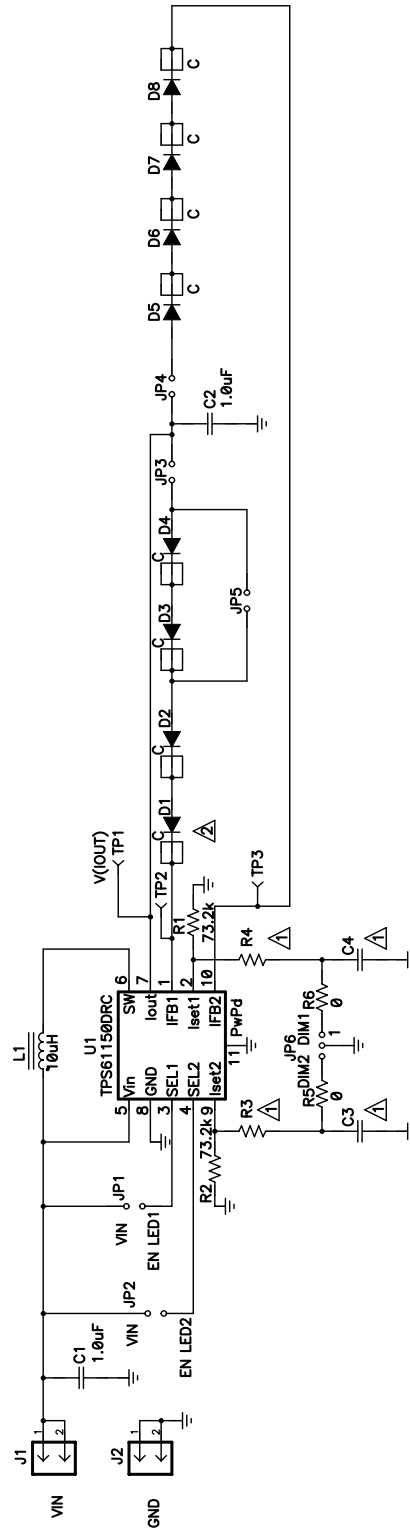


Figure 1. Schematic

3.1 Bill of Materials

Table 1. HPA150 Bill of Materials

| COUNT | REF DES | VALUE | DESCRIPTION | SIZE | PART NUMBER | MFR |
|-------|---------|-----------------|---|----------------------|------------------------------------|----------|
| 1 | C1 | 1.0 μ F | Capacitor, Ceramic, 25 V, X5R, 10% | 0603 | C1608X5R1E105K | TDK |
| 1 | C2 | 1.0 μ F | Capacitor, Ceramic, 50V, X7R, 10% | 1206 | C3216X7R1H105K | TDK |
| 2 | C3, C4 | Open | Capacitor, Ceramic, vvV | 0603 | | |
| 8 | D1–D8 | | Diode, LED, White, 30 mA, Common Anode | P-LCC-4 | Q65110A1931 LW E67C-U2V2-5K8L-1 | Osram |
| 2 | J1, J2 | | Header, 2-pin, 100 mil spacing, (36-pin strip) | 0.100 \times 2 | PTC36SAAN | Sullins |
| 5 | JP1–JP5 | | Header, 2-pin, 100 mil spacing, (36-pin strip) | 0.100 \times 2 | PTC36SAAN | Sullins |
| 1 | JP6 | | Header, 3-pin, 100 mil spacing, (36-pin strip) | 0.100 \times 3 | PTC36SAAN | Sullins |
| 1 | L1 | 10 μ H | Inductor, SMT, 1.26 A, 163 m Ω | 0.137 \times 0.147 | VLF4018AT-100MR74-2 | TDK |
| 2 | R1, R2 | 73.2 k Ω | Resistor, Chip, 1/16 W, 1% | 0603 | Std | Std |
| 2 | R3, R4 | Open | Resistor, Chip, 1/16 W | 0603 | | |
| 2 | R5, R6 | 0 | Resistor, Chip, 1/16 W, 1% | 0603 | Std | Std |
| 3 | TP1–TP3 | | Test Point, Red, Thru Hole Color Keyed | 0.100 x 0.100 | 5000 | Keystone |
| 1 | U1 | | IC, Dual Output Boost Regulator Using Single Inductor | DRC10 | TPS61150DRC | TI |
| 1 | – | | PCB, 1.95 In \times 1.55 In \times 0.062 In | | HPA150 | Any |
| 6 | – | | Shunt, 100-mil, Black | 0.100 | 929950-00 | 3M |

4 Using the TPS61150 in Other WLED and LCD Backlight Applications

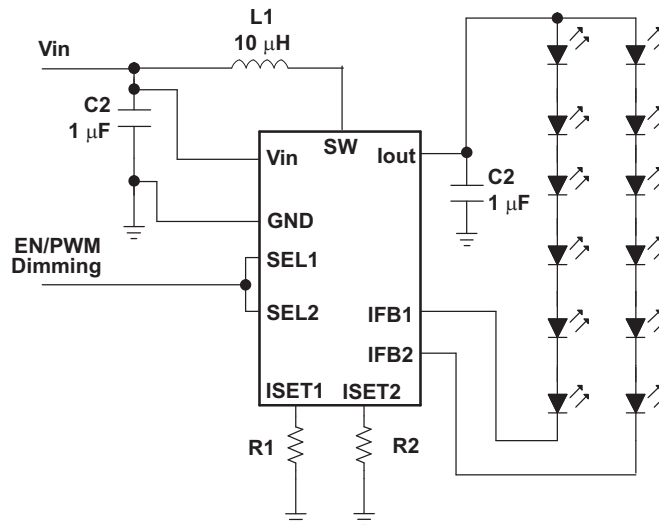


Figure 2. Driving Up to 14 WLEDs With One LCD Backlight

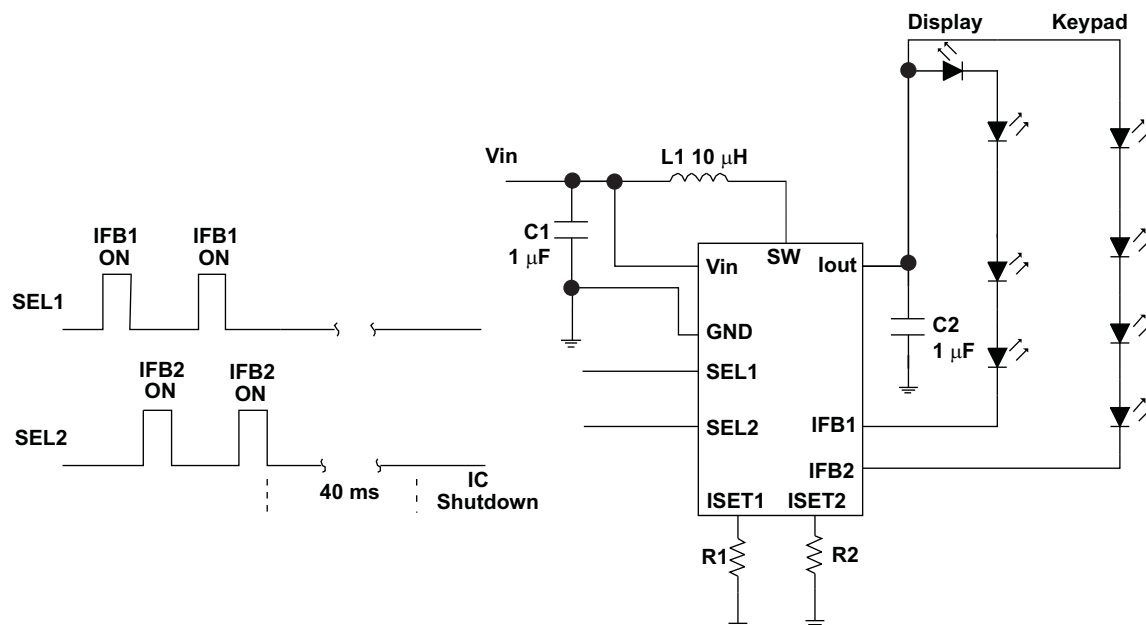


Figure 3. Driving a Keypad and LCD Backlight by applying interleaved PWM signal to the SEL1 and SEL2 pins. The duty cycle of the PWM signal controls brightness dimming

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

| Products | | Applications | |
|--------------------|--|---------------------|--|
| Amplifiers | amplifier.ti.com | Audio | www.ti.com/audio |
| Data Converters | dataconverter.ti.com | Automotive | www.ti.com/automotive |
| DSP | dsp.ti.com | Broadband | www.ti.com/broadband |
| Interface | interface.ti.com | Digital Control | www.ti.com/digitalcontrol |
| Logic | logic.ti.com | Military | www.ti.com/military |
| Power Mgmt | power.ti.com | Optical Networking | www.ti.com/opticalnetwork |
| Microcontrollers | microcontroller.ti.com | Security | www.ti.com/security |
| Low Power Wireless | www.ti.com/lpw | Telephony | www.ti.com/telephony |
| | | Video & Imaging | www.ti.com/video |
| | | Wireless | www.ti.com/wireless |

Mailing Address: Texas Instruments
Post Office Box 655303 Dallas, Texas 75265