

Operating the TPS61042 From Two Li-Ion and Input Voltages Higher Than 6 V

PMP Portable Power

ABSTRACT

The following designs show how to operate the TPS61042 switch boost converter from input voltages greater than 6 V.


1 Features

- Current Source With Overvoltage Protection
- Input Voltage Range . . 1.8 V to 6.0 V
- Internal 30 V Switch
- Up to 85% Efficiency
- Precise Brightness Control Using PWM Signal or Analog Signal
- Switching Frequency . . Up to 1 MHz
- Internal Power MOSFET Switch . . 500 mA
- Operates With Small Output Capacitors Down to 100 nF
- Disconnects LEDs During Shutdown
- No Load Quiescent Current . . 38 μ A Typ
- Shutdown Current . . 0.1 μ A Typ
- Available in a Small 3 mm \times 3 mm QFN Package

2 TPS61042 Reference Design

The reference design uses the TPS61042 high-efficiency boost converter and is configured to supply 20 mA of bias current to four white LEDs in series, from a 1.8-V to 6-V input voltage.


3 Schematic

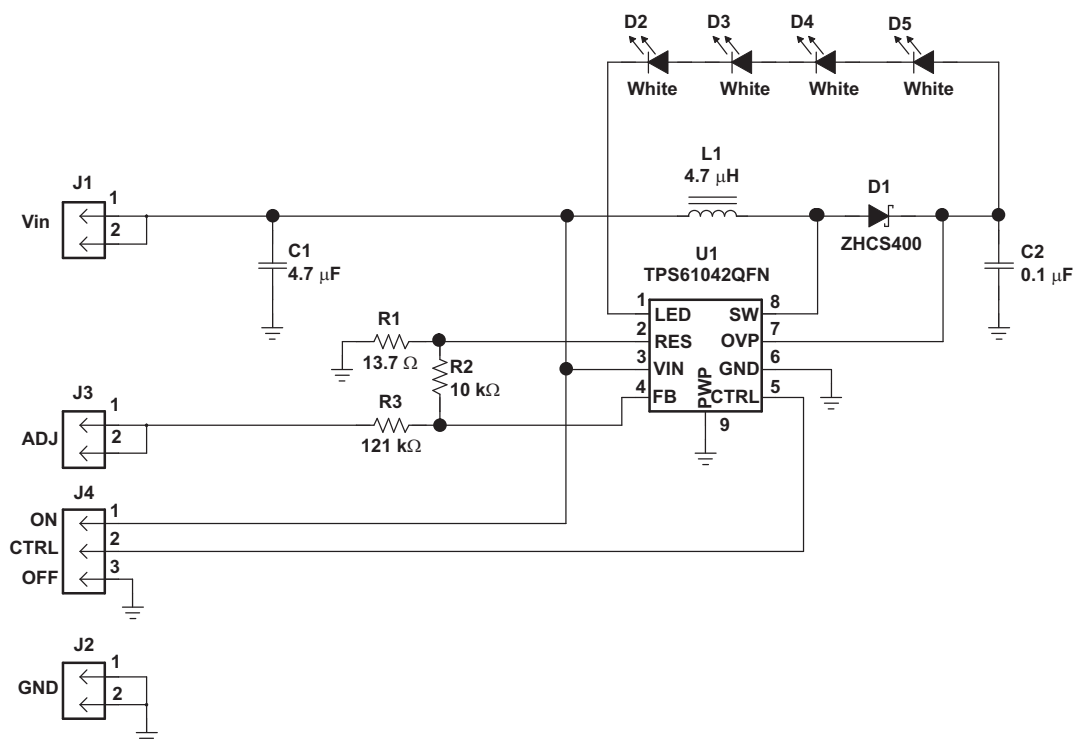


4 Bill of Material

Count	Ref Des	Description	Size	MFR	Part Number
1	C1	Capacitor, ceramic, 4.7 µF, 6.3 V, X5R, 10%	805	Murata	GRM21BR60J475KA1 1
1	C2	Capacitor, ceramic, 0.1 µF, 25 V, X7R, 10%	603	Murata	GRM188R71E104KA0 1
1	D1	Diode, Schottky, 400 mA, 40 V	SOD323	Zetex	ZHCS400
4	D2–D5	Diode, LED, white, 30 mA	1210	Lumex	SML-LX2832UWC-TR
3	J1–J3	Header, 2-pin, 100 mil spacing, (36-pin strip)	0.100 × 2	Sullins	PTC36SAAN
1	J4	Header, 3-pin, 100 mil spacing, (36-pin strip)	0.100 × 3	Sullins	PTC36SAAN
1	L1	Inductor, 4.7 µH, 750 mA, 216 mΩ	0.500 × 0.500	Sumida	CMD4D11-4R7
1	R1	Resistor, chip, 13.7 W, 1/16-W, 1%	603	Std	Std
1	R2	Resistor, chip, 10 kΩ, 1/16-W, 1%	603	Std	Std
1	R3	Resistor, chip, 121 kΩ, 1/16-W, 1%	603	Std	Std
1	U1	IC, LED driver	QFN-8P	TI	TPS61042QFN
1	—	PCB, 1.2 In × 1.05 In × 0.062 In		Any	SLVP226
1	—	Shunt, 100 mil, black	0.100	3M	929950-00

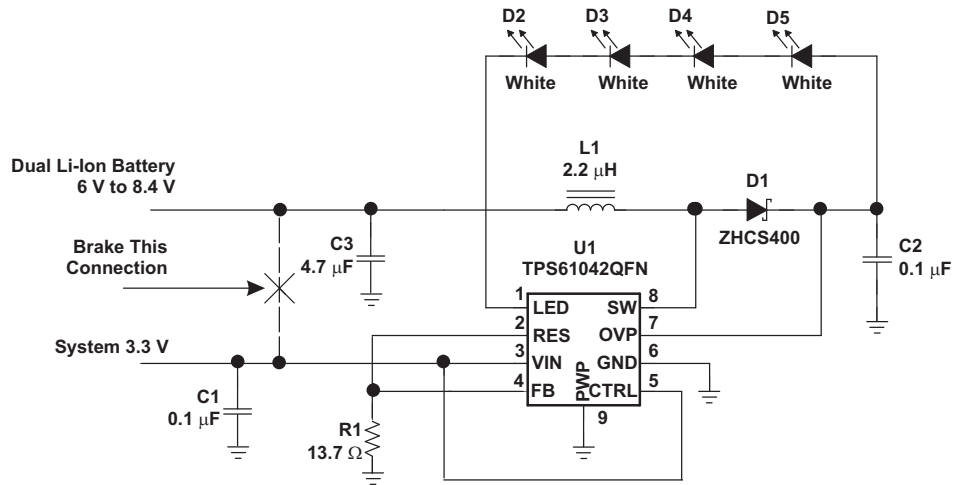5 Modified TPS61042 Design for Higher Input Voltages




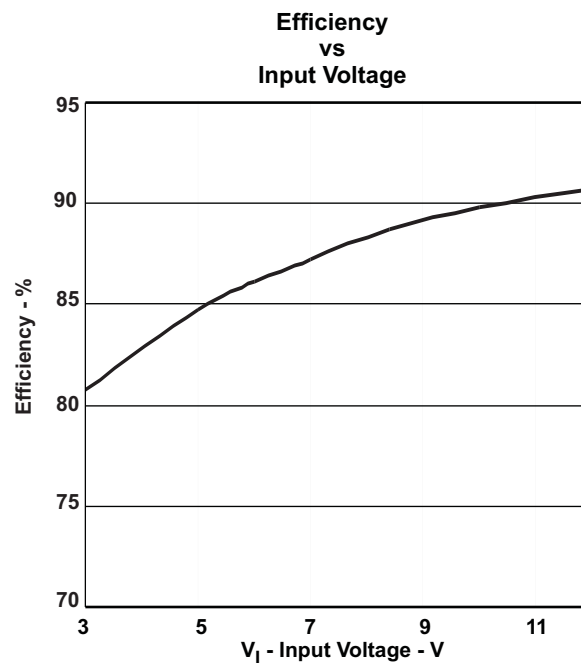This technique provides two additional benefits: increased efficiency and higher available power output. The following graph shows the increase in efficiency with rising input voltage for a typical four-white-LED application.



The increase in output power with increased input voltage is a function of the TPS61042 operating topology. The following graph shows the TPS61042 maximum drive current versus input voltage for a typical four-white-LED load drive circuit.

4 LED DRIVE CURRENT VS INPUT VOLTAGE

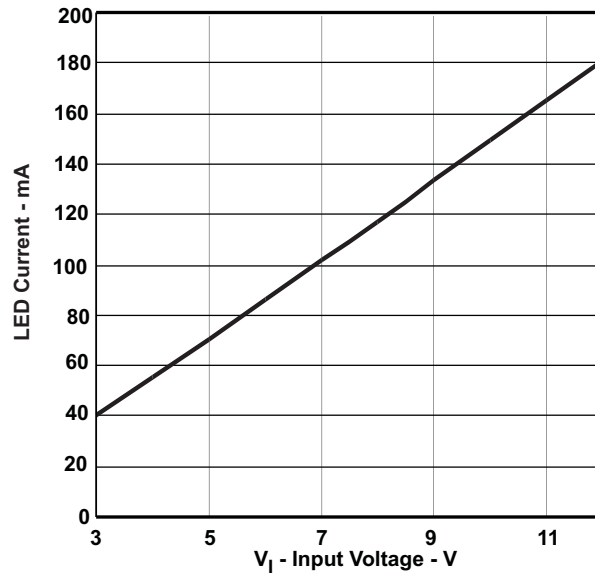

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products		Applications	
Amplifiers	amplifier.ti.com	Audio	www.ti.com/audio
Data Converters	dataconverter.ti.com	Automotive	www.ti.com/automotive
DSP	dsp.ti.com	Broadband	www.ti.com/broadband
Interface	interface.ti.com	Digital Control	www.ti.com/digitalcontrol
Logic	logic.ti.com	Military	www.ti.com/military
Power Mgmt	power.ti.com	Optical Networking	www.ti.com/opticalnetwork
Microcontrollers	microcontroller.ti.com	Security	www.ti.com/security
Low Power Wireless	www.ti.com/lpw	Telephony	www.ti.com/telephony
		Video & Imaging	www.ti.com/video
		Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments
Post Office Box 655303 Dallas, Texas 75265