
Using the TPS61150 with $V_{IN} > 6V$

Jeff Falin / Yunruo Yao

HPA Portable Power Management

ABSTRACT

This application note provides an example circuit of how to drive two strings of six wLEDs using the TPS61150 with a input voltage greater than the ICs 6-V absolute maximum voltage rating.

The TPS61150 is a boost converter used to regulate the current through wLEDs. In some applications needing wLEDs, a 3.0-V to 6.0-V voltage supply may be unavailable to power the TPS61150. In addition, reviewing equations 2 and 3 from the TPS61150 datasheet and recalling that boost converter efficiency improves as the input to output voltage differential decreases, it is apparent that higher output power, either as higher output current or higher output voltage (i.e., more wLEDs in series) is possible with a higher input voltage. [Figure 1](#) shows a circuit that uses the TPS61150 power stage to drive two strings of six wLEDs from an input supply greater than 6V.

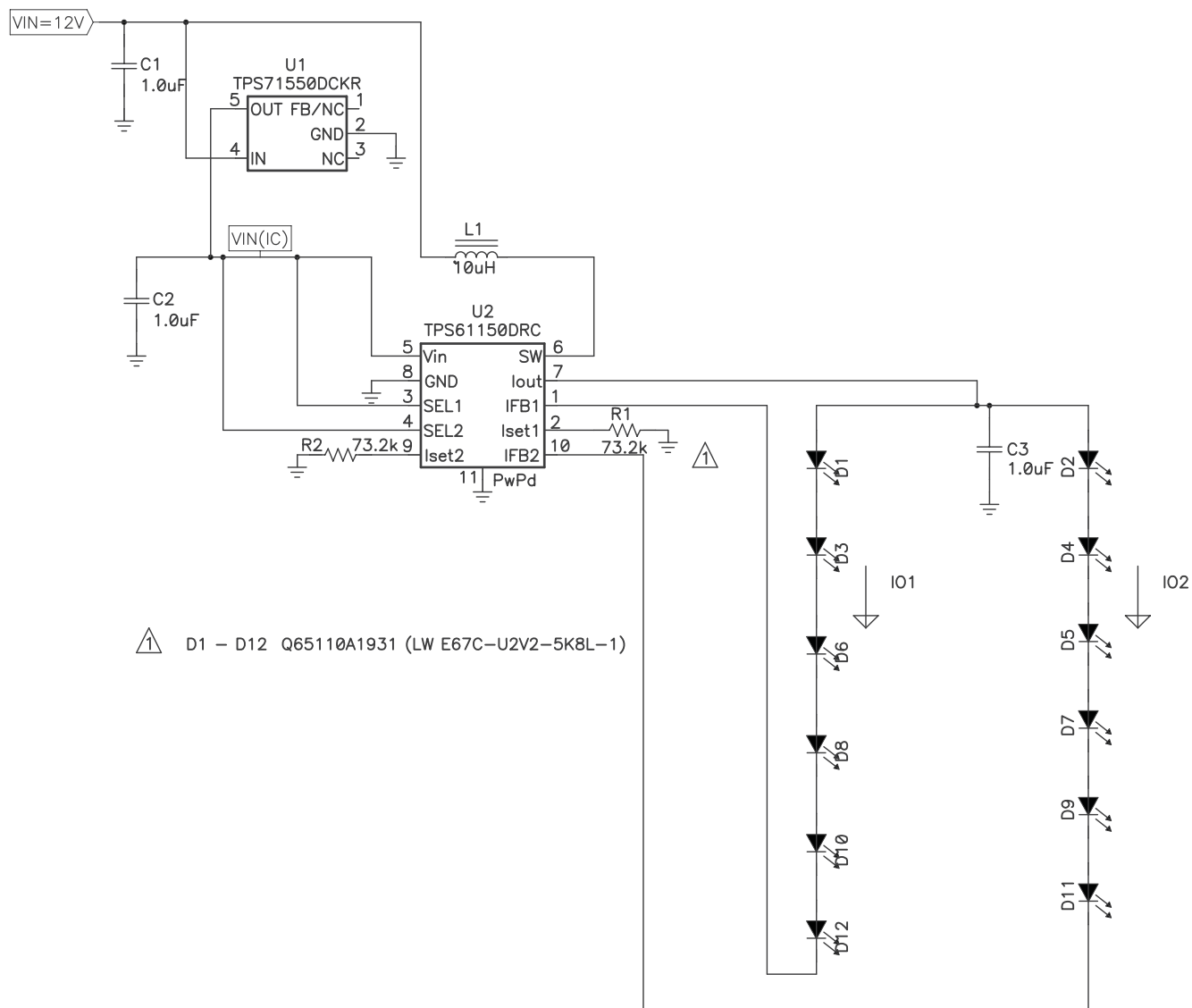


Figure 1. TPS61150 Driving 2×6 WLED Strings From $V_{IN} = 12V$

The TPS71550 linear regulator steps down the 12V input supply to power the TPS61150's control circuitry. Since the TPS61150 control circuitry operating current is typically 2 mA, power dissipation in the TPS71550 is not a concern up to $V_{IN} = 24V$, the linear regulator's maximum input voltage. Figure 2 shows peak efficiency over load with TPS61150 powering both strings of WLEDs from various input voltages.

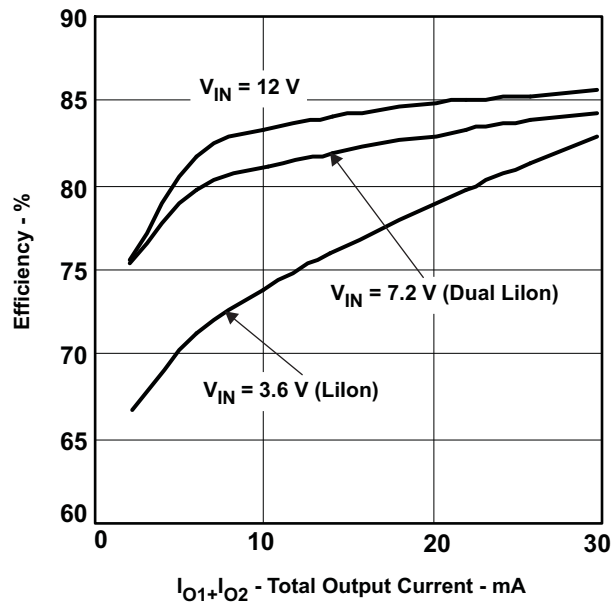


Figure 2. Both On Efficiency

The current through each wLED string is dimmed using PWM dimming at 1kHz on SEL1 and SEL2. Although the TPS61150 is capable of providing higher output currents, the maximum output current of the wLEDs used for the data in [Figure 2](#) was limited to less than about 15 mA per string.

The TPS71550 can be replaced by the slightly lower cost, discrete linear regulator shown in [Figure 3](#). However, most Zener diodes require current in the mA range to provide an accurate dc voltage so efficiency at light load suffers.

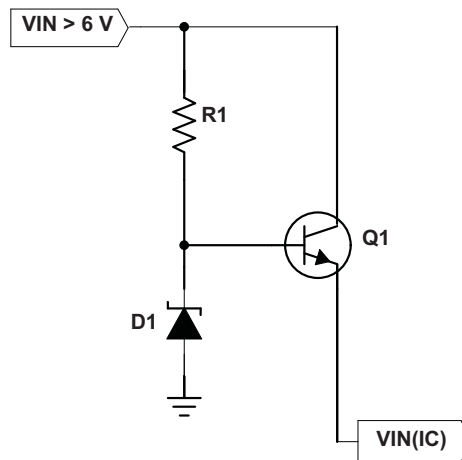


Figure 3. Discrete Linear Regulator

D1 should be a Zener diode with a clamp voltage of $V_Z = 6\text{ V}$ or less so that $V_{IN(IC)} = V_Z - V_{BE} < 6\text{ V}$, where V_{BE} is typically 0.6 V - 0.7 V. R1 is sized to provide the appropriate amount of bias current for D1. Q1 should have a breakdown voltage slightly higher than the maximum input voltage.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products		Applications	
Amplifiers	amplifier.ti.com	Audio	www.ti.com/audio
Data Converters	dataconverter.ti.com	Automotive	www.ti.com/automotive
DSP	dsp.ti.com	Broadband	www.ti.com/broadband
Interface	interface.ti.com	Digital Control	www.ti.com/digitalcontrol
Logic	logic.ti.com	Military	www.ti.com/military
Power Mgmt	power.ti.com	Optical Networking	www.ti.com/opticalnetwork
Microcontrollers	microcontroller.ti.com	Security	www.ti.com/security
Low Power Wireless	www.ti.com/lpw	Telephony	www.ti.com/telephony
		Video & Imaging	www.ti.com/video
		Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments
Post Office Box 655303 Dallas, Texas 75265