

TPS61060 Voltage Regulation Mode

Bill Johns

PMP Portable Power

ABSTRACT

The TPS61060, TPS61061, and TPS61062 are efficient white light-emitting diode (WLED) drivers. The standard mode of operation is to regulate a constant current through a string of WLEDs, but these ICs can also operate as a standard constant output voltage supply. This document shows the user how to configure the TPS6106x to generate a constant output voltage. It also provides guidelines on the application's capability and limitations.

1 Typical WLED Application

The typical TPS61060 configuration is current regulation. This is accomplished by using the Feedback pin (FB) to regulate a constant voltage across a current-sense resistor, R_s . The same current flows through the LEDs and through R_s . This current is calculated with [Equation 1](#):

$$I_{LED} = \frac{V_{fb}}{R_s} \tag{1}$$

Where V_{fb} is feedback voltage of the IC and R_s is the current-sense resistor. V_{fb} is user selectable to 0.25 V or 0.5 V by pulling ILED high or low. [Figure 1](#) shows the TPS61060 configured as a constant current driver. Connecting ILED to VIN sets the FB voltage to 0.25 V, which programs the LED current to 20.8 mA. Grounding the ILED sets the FB voltage to 0.5 V, which programs the LED current to 41.6 mA.

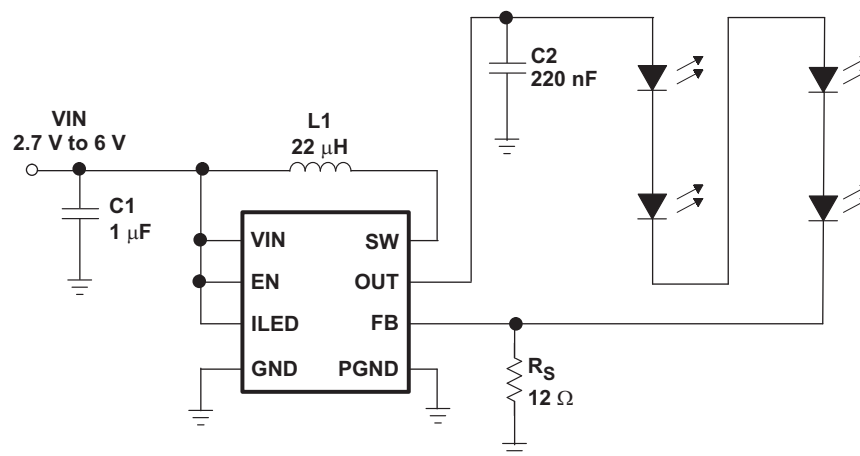


Figure 1. TPS6106x Configured as a Constant Current Driver

2 Voltage Regulation Application

To configure the TPS61060, TPS61061, or TPS61062 for voltage regulation, remove the current-sense resistor and connect the FB pin to a voltage divider that samples the output voltage. [Figure 2](#) show the TPS61060 configured as a standard 15-V boost converter.

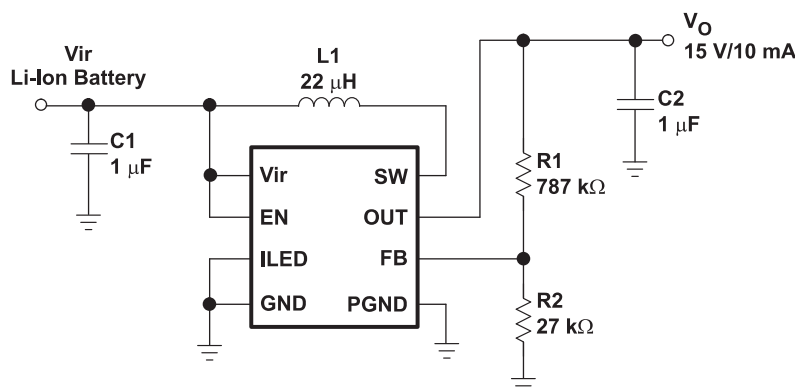


Figure 2. TPS6106x Configured as a Constant Voltage Regulator

Circuit performance and capability is similar to driving four WLEDs at 10 mA to 20 mA. The maximum output voltage is limited by each IC's overvoltage protection as the following shows:

TPS61060 — 14 V

TPS61061 — 18 V

TPS61062 — 22 V

The output voltage is calculated with the [Equation 2](#)

$$V_{out} = (V_{fb}) \times \left(\frac{R1 + R2}{R2} \right) \quad (2)$$

Where V_{fb} is the FB voltage, $R1$ is the top resistor divider, and $R2$ is the bottom resistor divider. Note that pulling ILED to ground sets $FB=0.5$ V and pulling ILED to V_{IN} sets $FB=0.25$ V. The best circuit performance is realized by grounding ILED. This improves noise immunity and reduces the output voltage set-point error caused by variations in $R1$ and $R2$.

Typical inductor and capacitor values identified in the data sheet provide good voltage regulation, 22 μ H and 1 μ F. Lower inductor values with a larger output capacitor improve transient performance; the lowest recommended inductor value is 4.7 μ H. See the [SLVS538](#) data sheet Equations 1, 2, and 3 for maximum output current and inductor peak current calculations.

Additional transient performance improvement can be achieved with a feedforward capacitance placed between V_{out} and FB pin. Maximum recommended value is 150 pF. [Figure 4](#) shows transient performance with inductor value of 4.7 μ H, output capacitor of 1 μ F, and a feedforward capacitor of 150 pF.

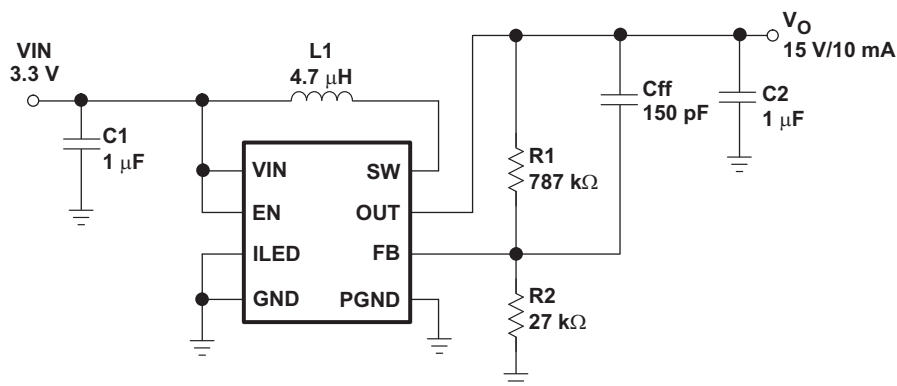


Figure 3. Improved Transient Response Circuit

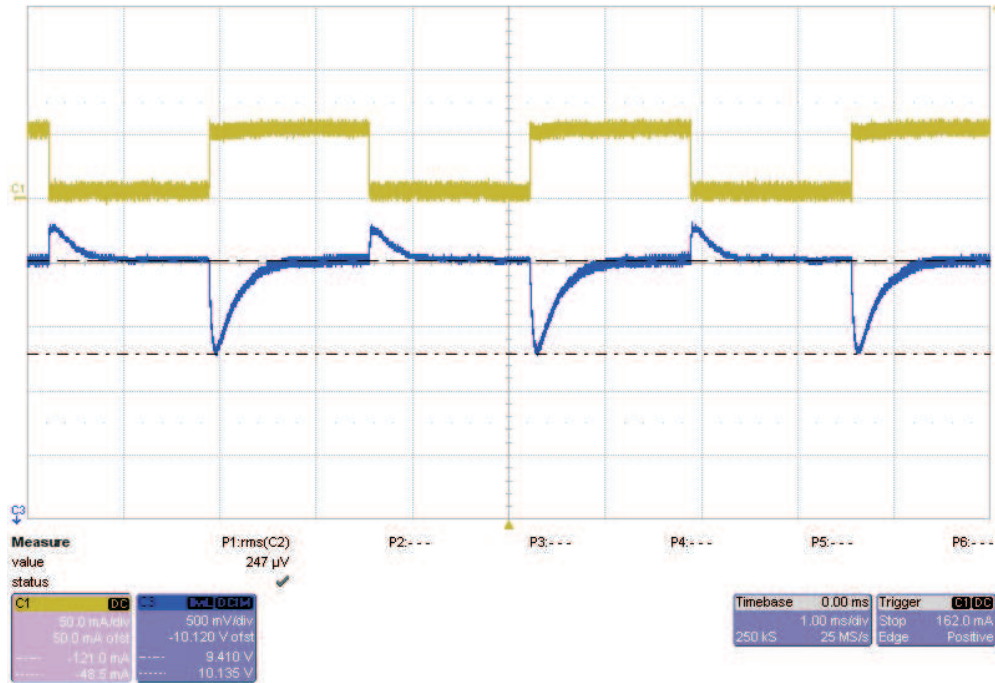


Figure 4. Load Transient 5 mA to 10 mA.
Output Voltage Overshoot +250 mV and -750 mV

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products		Applications	
Amplifiers	amplifier.ti.com	Audio	www.ti.com/audio
Data Converters	dataconverter.ti.com	Automotive	www.ti.com/automotive
DSP	dsp.ti.com	Broadband	www.ti.com/broadband
Interface	interface.ti.com	Digital Control	www.ti.com/digitalcontrol
Logic	logic.ti.com	Military	www.ti.com/military
Power Mgmt	power.ti.com	Optical Networking	www.ti.com/opticalnetwork
Microcontrollers	microcontroller.ti.com	Security	www.ti.com/security
Low Power Wireless	www.ti.com/lpw	Telephony	www.ti.com/telephony
		Video & Imaging	www.ti.com/video
		Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments
Post Office Box 655303 Dallas, Texas 75265